

# **Project 71: Sub-threshold Comparator**

**A Comprehensive Study of Advanced Digital Circuits**

**By: Nikunj Agrawal , Gati Goyal, Abhishek Sharma , Ayush Jain**

**Documentation Specialist: Dhruv Patel & Nandini Maheshwari**

Created By Team Alpha

# Contents

<b>1 Introduction</b>	<b>3</b>
<b>2 Background</b>	<b>3</b>
<b>3 Structure and Operation</b>	<b>3</b>
3.1 Structure . . . . .	3
3.2 Operation . . . . .	3
<b>4 Implementation in System Verilog</b>	<b>4</b>
<b>5 Simulation Results</b>	<b>4</b>
<b>6 Test Bench</b>	<b>4</b>
<b>7 Advantages and Disadvantages</b>	<b>5</b>
7.1 Advantages . . . . .	5
7.2 Disadvantages . . . . .	5
<b>8 Schematic</b>	<b>6</b>
<b>9 Synthesis Design</b>	<b>6</b>
<b>10 Conclusion</b>	<b>7</b>
<b>11 Frequently Asked Questions (FAQs)</b>	<b>7</b>
11.1 1. What is a sub-threshold comparator? . . . . .	7
11.2 2. How does a sub-threshold comparator work? . . . . .	7
11.3 3. What are the common applications of sub-threshold comparators? . . . . .	7
11.4 4. What are the advantages of sub-threshold comparators? . . . . .	7
11.5 5. What are the limitations of sub-threshold comparators? . . . . .	7
11.6 6. How do sub-threshold comparators differ from other types of comparators? . . . . .	7

# 1 Introduction

Sub-threshold comparators are critical components in low-power applications, particularly in battery-operated devices and energy-efficient systems. These comparators operate in the sub-threshold region of MOSFETs, where the transistor is biased below the threshold voltage, allowing for significant reductions in power consumption while maintaining sufficient performance for specific applications.

The design of sub-threshold comparators leverages the unique characteristics of MOSFETs in the sub-threshold region, enabling them to achieve low voltage operation and high sensitivity. This document provides an overview of sub-threshold comparators, detailing their architecture, operation, advantages, and applications.

## 2 Background

Sub-threshold comparators function by utilizing the exponential relationship between the gate voltage and the drain current in MOSFETs operating in the sub-threshold region. This behavior allows for precise voltage comparisons with minimal power consumption.

The key feature of sub-threshold comparators is their ability to function effectively at low supply voltages, making them suitable for modern low-power digital systems. This document will explore the various components and operational phases of sub-threshold comparators in detail.

## 3 Structure and Operation

Sub-threshold comparators consist of several essential components that enable their efficient operation.

### 3.1 Structure

The structure of a sub-threshold comparator typically includes:

- **Input Transistors:** Differential pairs of NMOS or PMOS transistors that operate in the sub-threshold region.
- **Current Mirror:** A current mirror circuit to bias the differential pair, providing a stable reference current.
- **Latch Circuit:** Feedback latches that hold the output state once a comparison is made.
- **Output Stage:** A buffer or inverter to convert the differential output to a single-ended signal.

### 3.2 Operation

The operation of a sub-threshold comparator can be broken down into several phases:

1. **Input Sampling:** The input voltages are applied to the differential pairs, and the comparator samples the input signals.
2. **Evaluation Phase:** During this phase, the comparator evaluates which input is greater based on the sub-threshold current characteristics.
3. **Latching Phase:** The output is latched to maintain the result of the comparison. This ensures that the output state is stable until the next evaluation cycle.
4. **Reset Phase:** After the output is stable, the circuit resets to prepare for the next comparison cycle.

The operation in the sub-threshold region allows the comparator to achieve low power consumption while still providing reliable performance.

## 4 Implementation in System Verilog

Below is an example of a simple sub-threshold comparator implemented in System Verilog:

Listing 1: Sub-threshold Comparator

```
1 module SubThresholdComparator (
2     input logic [3:0] a,           // Input A
3     input logic [3:0] b,           // Input B
4     output logic a_gt_b,           // Output: A > B
5     output logic a_eq_b,           // Output: A == B
6     output logic a_lt_b            // Output: A < B
7 );
8     always_comb begin
9         a_gt_b = (a > b);
10        a_eq_b = (a == b);
11        a_lt_b = (a < b);
12    end
13 endmodule
```

## 5 Simulation Results

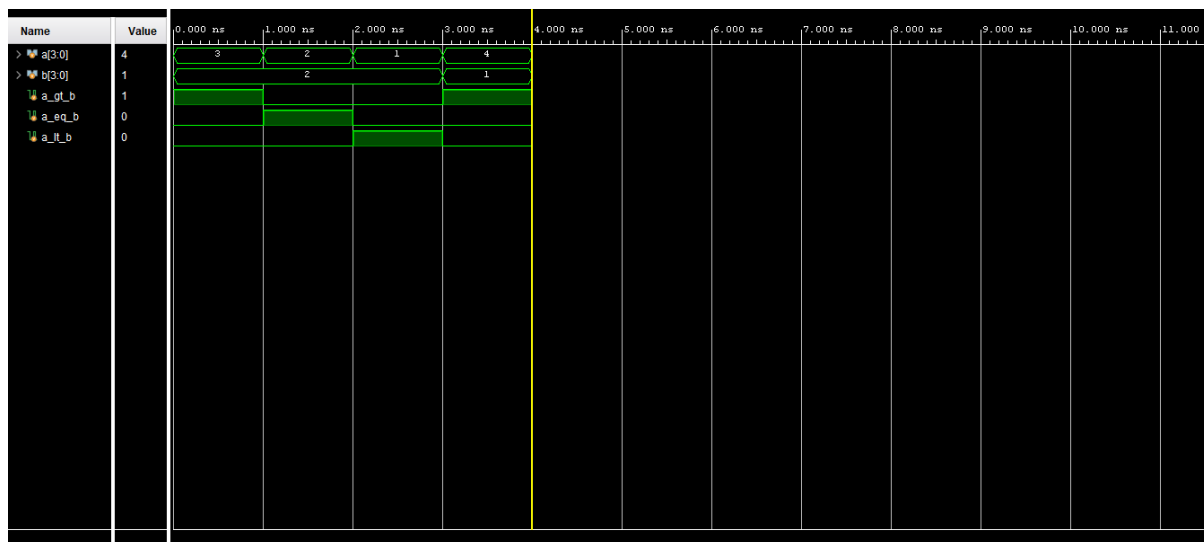


Figure 1: Simulation results of Sub-threshold Comparator

## 6 Test Bench

The following test bench verifies the functionality of the sub-threshold comparator:

Listing 2: Sub-threshold Comparator Testbench

```
1 module tb_SubThresholdComparator;
2     logic [3:0] a;
3     logic [3:0] b;
4     logic a_gt_b;
5     logic a_eq_b;
6     logic a_lt_b;
7
8     SubThresholdComparator uut (
```

```

9      .a(a),
10     .b(b),
11     .a_gt_b(a_gt_b),
12     .a_eq_b(a_eq_b),
13     .a_lt_b(a_lt_b)
14 );
15
16 initial begin
17     // Test Case 1: A = 3, B = 2
18     a = 4'd3; b = 4'd2;
19     #1; // Wait for combinational logic to settle
20     assert(a_gt_b && !a_eq_b && !a_lt_b) else $fatal("Test Case 1
        Failed");
21
22     // Test Case 2: A = 2, B = 2
23     a = 4'd2; b = 4'd2;
24     #1; // Wait for combinational logic to settle
25     assert(!a_gt_b && a_eq_b && !a_lt_b) else $fatal("Test Case 2
        Failed");
26
27     // Test Case 3: A = 1, B = 2
28     a = 4'd1; b = 4'd2;
29     #1; // Wait for combinational logic to settle
30     assert(!a_gt_b && !a_eq_b && a_lt_b) else $fatal("Test Case 3
        Failed");
31
32     // Test Case 4: A = 4, B = 1
33     a = 4'd4; b = 4'd1;
34     #1; // Wait for combinational logic to settle
35     assert(a_gt_b && !a_eq_b && !a_lt_b) else $fatal("Test Case 4
        Failed");
36
37     // Finish simulation
38     $finish;
39 end
40 endmodule

```

## 7 Advantages and Disadvantages

Sub-threshold comparators offer several advantages and disadvantages that impact their application in electronic systems.

### 7.1 Advantages

- **Ultra-Low Power:** Operating in the sub-threshold region allows for significantly reduced power consumption.
- **Low Voltage Operation:** They can operate effectively at low supply voltages, making them suitable for portable devices.
- **High Sensitivity:** The exponential relationship of sub-threshold operation provides high sensitivity in voltage comparisons.

### 7.2 Disadvantages

- **Speed Limitations:** Sub-threshold comparators may operate slower than standard comparators due to reduced drive current.

- **Temperature Sensitivity:** Performance can be affected by temperature variations, requiring careful design considerations.
- **Limited Input Range:** The input voltage range may be constrained due to the sub-threshold operation.

## 8 Schematic

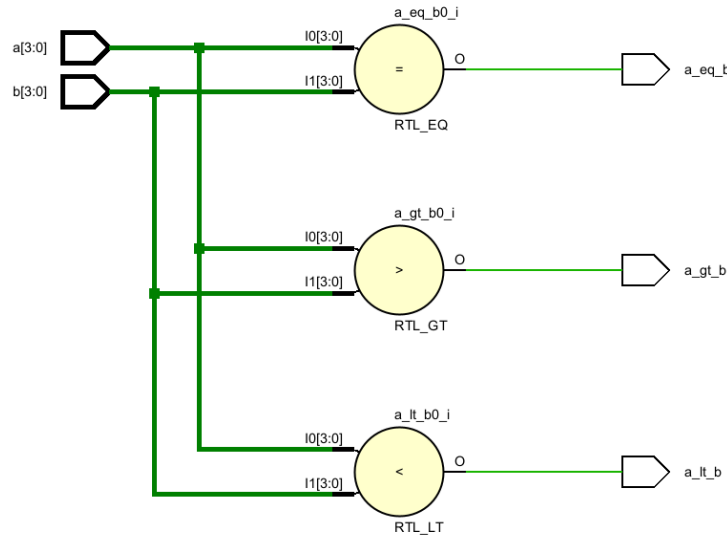


Figure 2: Schematic of Sub-threshold Comparator

## 9 Synthesis Design

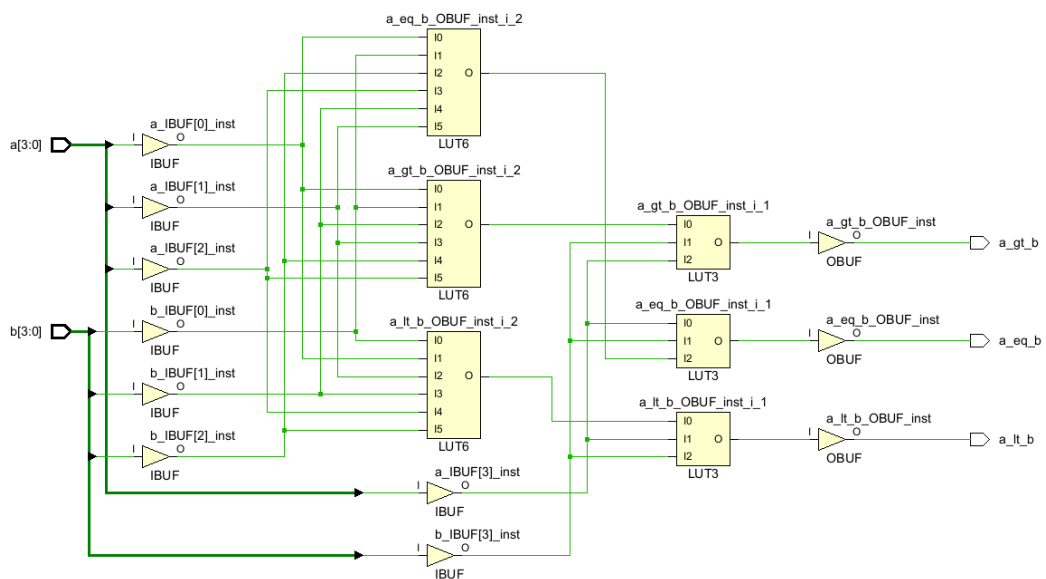


Figure 3: Synthesis of Sub-threshold Comparator

## 10 Conclusion

Sub-threshold comparators are essential components in modern low-power electronic systems. Their ability to function at low voltages while providing high sensitivity makes them ideal for applications in portable and energy-efficient devices.

As technology advances, sub-threshold comparators will continue to evolve, driving innovations in low-power design and expanding their applications in various fields. Understanding their design and operational principles is crucial for engineers working in low-power electronics.

## 11 Frequently Asked Questions (FAQs)

### 11.1 1. What is a sub-threshold comparator?

A sub-threshold comparator is a circuit that compares two input voltages while operating in the sub-threshold region of MOSFETs, enabling low power consumption.

### 11.2 2. How does a sub-threshold comparator work?

Sub-threshold comparators leverage the exponential current-voltage characteristics of MOSFETs in the sub-threshold region to perform voltage comparisons efficiently.

### 11.3 3. What are the common applications of sub-threshold comparators?

Common applications include:

- Low-Power Analog-to-Digital Converters (ADCs)
- Energy-Efficient Signal Processing Circuits
- Battery-Powered Devices

### 11.4 4. What are the advantages of sub-threshold comparators?

Advantages include ultra-low power operation, low voltage functionality, and high sensitivity.

### 11.5 5. What are the limitations of sub-threshold comparators?

Limitations may include speed constraints, temperature sensitivity, and a limited input voltage range.

### 11.6 6. How do sub-threshold comparators differ from other types of comparators?

Sub-threshold comparators operate in a lower voltage range and consume less power compared to standard comparators, making them suitable for specific low-power applications.