

Project 78: Programmable Shifter

A Comprehensive Study of Advanced Digital Circuits

By: Gati Goyal, Nikunj Agrawal, Abhishek Sharma, Ayush Jain

Documentation Specialist: Dhruv Patel, Nandini Maheshwari

Created By team alpha

Contents

1	Introduction	3
2	Key Concepts of Programmable Shifter	3
2.1	1. Shift Direction	3
2.2	2. Shift Amount	3
2.3	3. Data Width	3
2.4	4. Logic Implementation	3
2.5	5. Applications	3
3	Steps in Programmable Shifter	3
4	Reasons to Choose Programmable Shifter	4
5	SystemVerilog Code	4
6	Testbench	5
7	Conclusion	7
8	References	7
9	FAQs for Programmable Shifter	8

Created By team alpha

1 Introduction

A Programmable Shifter is a digital circuit that shifts binary data left or right by a specified number of positions based on control signals. It supports both left and right shifts, enabling data manipulation for applications like efficient multiplication/division, data alignment, and bit masking. By allowing the shift amount to be programmable, it offers flexibility for various computational tasks in digital systems.

2 Key Concepts of Programmable Shifter

2.1 1. Shift Direction

- Controls the direction of data shifting, either to the left or right.
- Left shift generally multiplies data by powers of two, while right shift divides it.

2.2 2. Shift Amount

- Specifies the number of bit positions for the data shift.
- Programmable to allow flexibility for different applications.

2.3 3. Data Width

- Defines the width (in bits) of the data input and output, such as 8-bit or 16-bit.
- Determines the range of values the shifter can handle.

2.4 4. Logic Implementation

- Uses combinational logic for immediate response based on inputs.
- Processes shift direction and amount to produce output without delay.

2.5 5. Applications

- Commonly used in arithmetic operations, like multiplication and division by powers of two.
- Widely applied in digital signal processing and data alignment tasks.
- Essential in systems requiring efficient data manipulation, like encryption and compression.

3 Steps in Programmable Shifter

1. Define Requirements:

- Determine the specifications such as the number of bits to shift, shift direction (left or right), and types of shifts needed (logical, arithmetic, circular).

2. Select Architecture:

- Choose an appropriate architecture based on multiplexers, registers, or combinational logic circuits.

3. Design Control Logic:

- Develop the control logic that manages the shifting process, including binary encoding for shift amount and direction.

4. Implement Shift Functionality:

- Create the shift operations using logic gates or multiplexers to adjust the position of bits based on control signals.

5. Integrate Input and Output:

- Design the input interface to accept data for shifting and the output interface to provide the shifted data.

6. Testing and Verification:

- Simulate the design to verify functionality and confirm expected behavior with various shift amounts and directions.

7. Optimization:

- Analyze the design for speed, area, and power consumption, making necessary optimizations.

8. Hardware Implementation:

- Implement the design on a physical platform (FPGA or ASIC) and integrate it into the larger system.

9. Final Testing:

- Perform comprehensive testing on the hardware to ensure it meets specifications and operates reliably.

10. Documentation:

- Document the design, including schematics, logic diagrams, and test results for future reference.

4 Reasons to Choose Programmable Shifter

- **Versatility:** A programmable shifter provides the ability to perform multiple types of shifts (e.g., logical, arithmetic, circular) in both left and right directions, making it suitable for a wide range of applications.
- **Efficient Data Manipulation:** It allows for efficient bit manipulation in digital systems, which is essential in tasks such as data compression, cryptography, and signal processing.
- **Enhanced Processing Speed:** By providing built-in shifting capabilities, programmable shifters reduce the need for additional logic, allowing data to be processed faster and with lower latency.
- **Power Efficiency:** Programmable shifters optimize operations by minimizing the need for external components or complex circuitry, leading to reduced power consumption.
- **Scalability:** Programmable shifters can be scaled in design to accommodate different word sizes or bit widths, providing flexibility in integration within larger digital systems.
- **Ease of Integration:** These shifters are easy to implement in standard CMOS technology and can be integrated seamlessly into various digital circuits or processors.

5 SystemVerilog Code

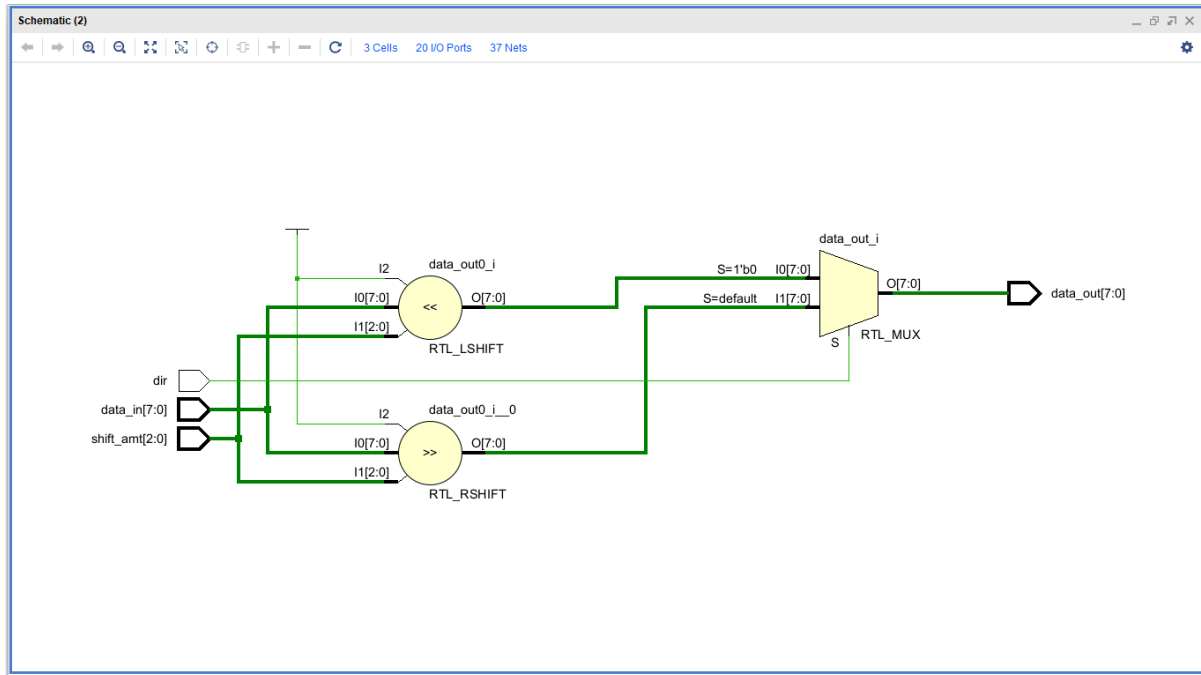


Figure 1: Schematic of Programmable Shifter

Listing 1: Programmable Shifter RTL Code

```

1 module programmable_shifter #(
2     parameter WIDTH = 8 // Width of the data
3 ) (
4     input logic [WIDTH-1:0] data_in, // Input data to be shifted
5     input logic [2:0] shift_amt, // Shift amount (3 bits for
6         up to 7 shifts)
7     input logic dir, // Direction: 0 for left, 1
8         for right
9     output logic [WIDTH-1:0] data_out // Output data after shift
10 );
11
12 always_comb begin
13     if (dir == 1'b0) // Left shift
14         data_out = data_in << shift_amt;
15     else // Right shift
16         data_out = data_in >> shift_amt;
17 end
18 endmodule

```

6 Testbench

Listing 2: Programmable Shifter Testbench

```

1 module tb_programmable_shifter();
2
3     parameter WIDTH = 8;
4     logic [WIDTH-1:0] data_in;
5     logic [2:0] shift_amt;
6     logic dir;
7     logic [WIDTH-1:0] data_out;
8

```

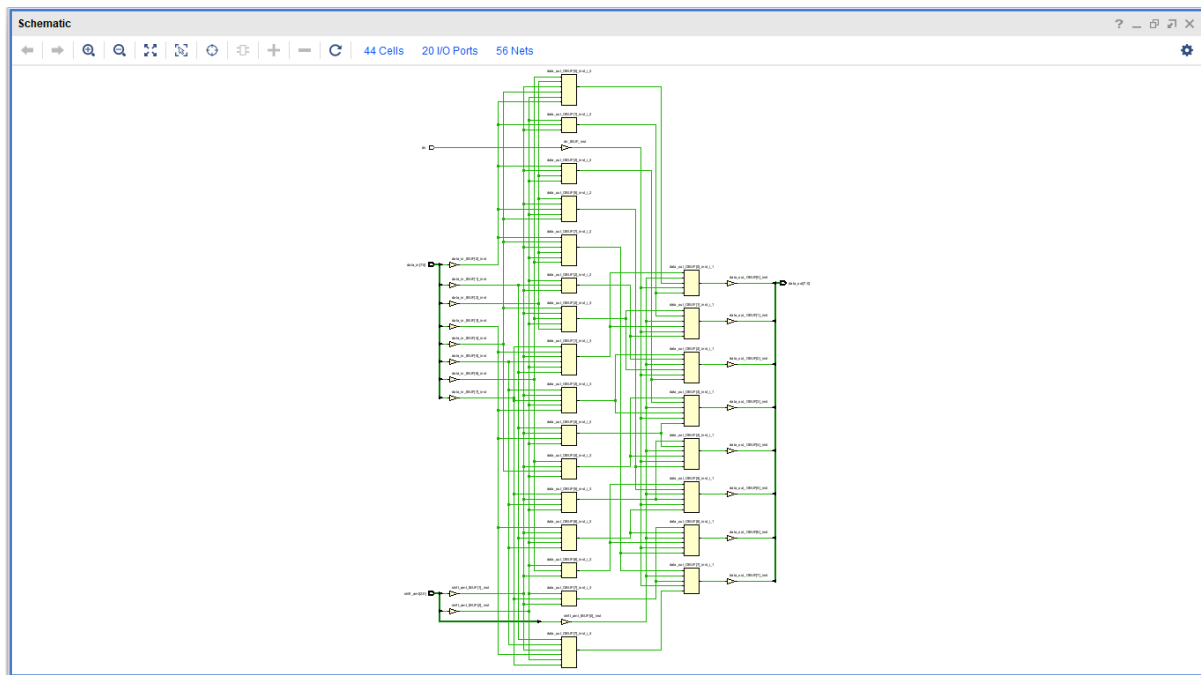


Figure 2: Synthesis of Programmable Shifter

```

9      // Instantiate the programmable shifter
10     programmable_shifter #(WIDTH) uut (
11         .data_in(data_in),
12         .shift_amt(shift_amt),
13         .dir(dir),
14         .data_out(data_out)
15     );
16
17     // Test process
18     initial begin
19         // Test case 1: Left shift by 1
20         data_in = 8'b0001_1101;
21         shift_amt = 3'b001; // Shift by 1
22         dir = 1'b0; // Left shift
23         #10;
24         $display("Test case 1 - Left Shift by 1: data_in = %b,
25                 data_out = %b", data_in, data_out);
26
27         // Test case 2: Right shift by 2
28         data_in = 8'b1110_0101;
29         shift_amt = 3'b010; // Shift by 2
30         dir = 1'b1; // Right shift
31         #10;
32         $display("Test case 2 - Right Shift by 2: data_in = %b,
33                 data_out = %b", data_in, data_out);
34
35         // Test case 3: Left shift by 3
36         data_in = 8'b0101_0101;
37         shift_amt = 3'b011; // Shift by 3
38         dir = 1'b0; // Left shift
39         #10;
40         $display("Test case 3 - Left Shift by 3: data_in = %b,
41                 data_out = %b", data_in, data_out);

```


3. Raghunandan, K. S., & Kothari, M. A. (2013). Design of a Programmable Shift Register Using Multiplexer and D Flip-Flop. *International Journal of Engineering Research Technology (IJERT)*, 2(3), 1-4.
4. Kher, N. S. H., & Ali, A. S. Z. (2013). A 4-Bit Programmable Shifter Using FPGA. *International Journal of Engineering Trends and Technology (IJETT)*, 4(2), 92-95.
5. Allstot, D. J., et al. (2005). A High-Performance CMOS Programmable Shifter. In *Proceedings of the IEEE International Symposium on Circuits and Systems* (pp. 123-126).
6. Electronics Tutorials. (n.d.). Shift Register. Retrieved from <https://www.electronicwings.com/>
7. All About Circuits. (n.d.). Digital Logic Design. Retrieved from <https://www.allaboutcircuits.com/textbook/digital/chpt-7/>

9 FAQs for Programmable Shifter

1. What is a programmable shifter?

A programmable shifter is a digital circuit that can shift binary data left or right by a variable number of positions based on control signals. It is often used in arithmetic operations and data manipulation in digital systems.

2. What are the applications of a programmable shifter?

Programmable shifters are widely used in various applications, including digital signal processing, data routing, arithmetic operations, and in the design of arithmetic logic units (ALUs) within microprocessors.

3. How does a programmable shifter differ from a regular shifter?

Unlike a regular shifter, which typically has fixed shift amounts and directions, a programmable shifter can be configured to shift data by any specified number of bits and in either direction (left or right) based on external control signals.

4. What types of shifts can a programmable shifter perform?

A programmable shifter can perform various types of shifts, including logical shifts (inserting zeros), arithmetic shifts (preserving the sign bit for signed numbers), and circular shifts (rotating bits around).

5. What are the benefits of using a programmable shifter?

Benefits include flexibility in handling different data formats, efficiency in performing multiplication and division through shifts, reduced circuit complexity, and improved speed and power efficiency.

6. How is a programmable shifter implemented in hardware?

Programmable shifters can be implemented using multiplexers, registers, and combinational logic circuits. The design often involves using FPGA or ASIC technology to allow for programmability.

7. What control signals are required for a programmable shifter?

Control signals typically include the direction of the shift (left or right) and the number of positions to shift, often represented in binary form.

8. Can a programmable shifter handle signed and unsigned numbers?

Yes, a programmable shifter can be designed to handle both signed and unsigned numbers, with specific configurations for arithmetic shifts to ensure correct handling of sign bits.

9. What is the impact of using a programmable shifter on circuit speed?

Programmable shifters can enhance circuit speed by performing shifts in a single clock cycle, which is generally faster than performing multiplication or division using traditional arithmetic circuits.

10. Are there any limitations to programmable shifters?

Limitations may include increased complexity in design, potential for larger circuit area due to added programmability features, and possible impacts on timing due to the need for additional control logic.